

# Handwritten Notes On Digital Electronics



# Digital Electronics


A Digital Electronics or Digital circuit operate with Binary Number & in Binary Number. there exist only two states which is either "zero" or "one".

- In +ve logic system Binary number 1 represent high state & 0 represent low state.
- In -ve logic system Binary Number 0 represent high state & 1 represent low state.
- In digital circuit the various circuit perform operation by counting digit.

## Logic Gate :

The circuits which are used to provide logical output, are k/as "Logic Gate".

# Transistor-Transistor Logic (TTL)

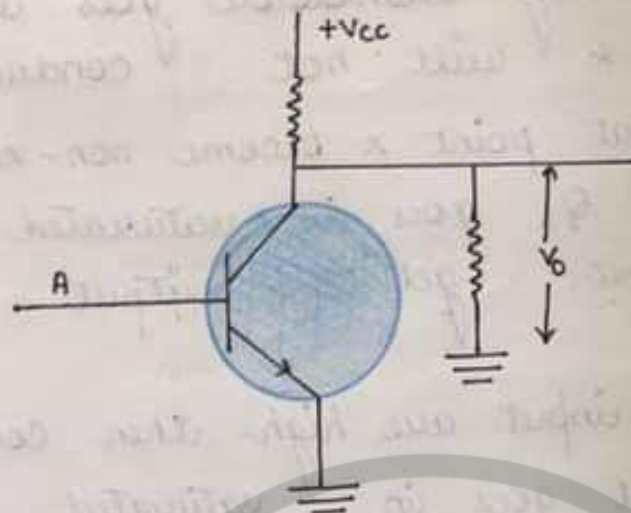


If input A is in low state then transistor goes in cutoff region & we get high output. If input is in high state then transistor goes in saturated region & we get low output.

NOT Gate work as Inverter.
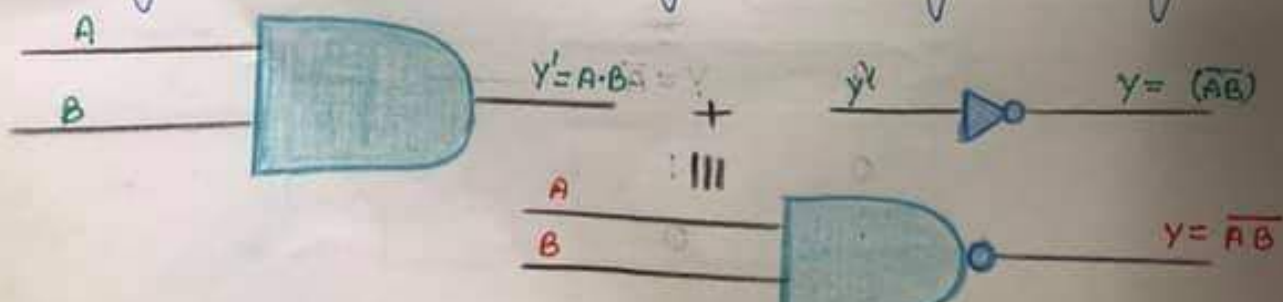
## • NAND Gate:

NAND Gate is a combination of NOT - AND gate. It has two or more input & only single output. So, logic symbol for NAND gate is given by;






## Truth Table:

A	B	AB	$Y = \overline{AB}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

According to De Morgan's Theorem the complement of a product is equal to the sum of complements. If A & B are input variables then, according to De Morgan's theorem,

$$\overline{AB} = \overline{A} + \overline{B}$$


A	B	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

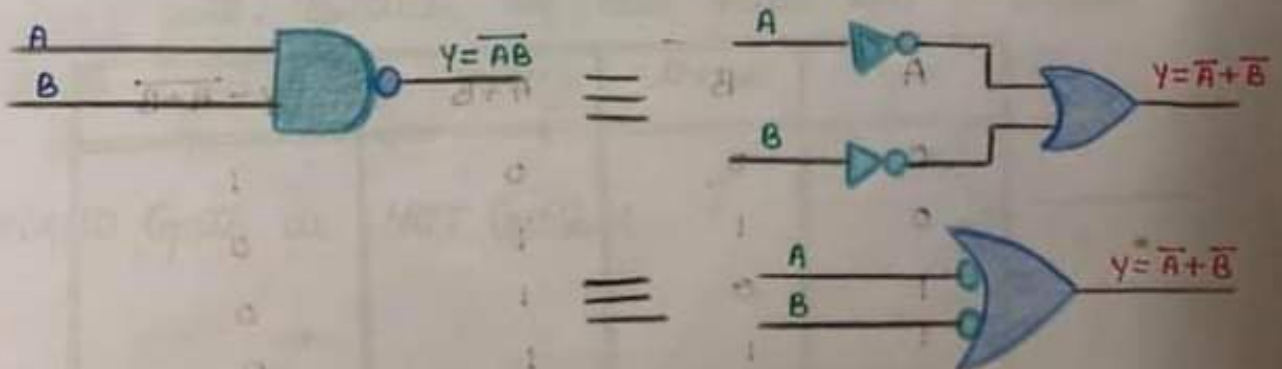

NAND Gate  $\equiv$  Bubbled OR Gate : dot AND

• NOR Gate:

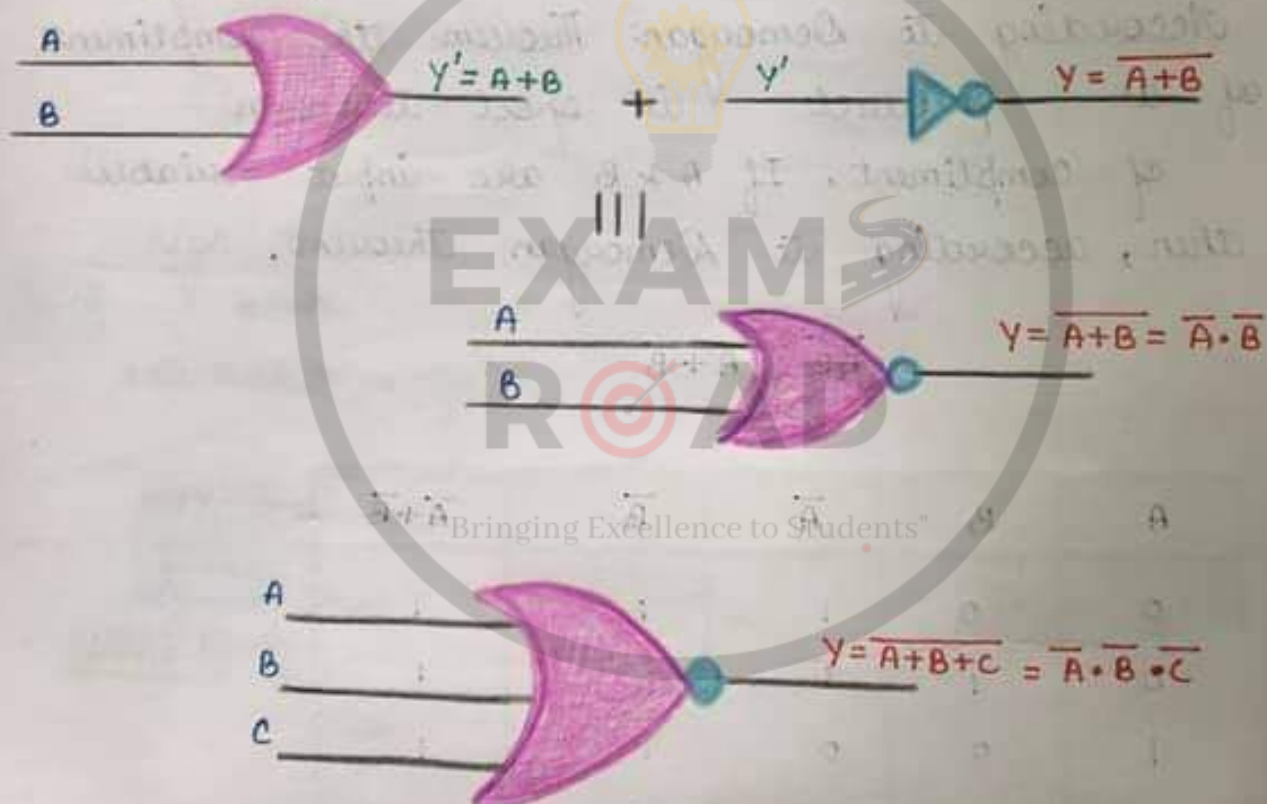NOR gate is a combination of NOT - OR gate it has two or more input but have only single output if A & B are input variable then logic symbol can be express as;



Truth Table:

A	B	A+B	$Y = \overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0






According to De-Morgan Theorem

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$


A	B	$\overline{A}$	$\overline{B}$	$Y = \overline{A} \cdot \overline{B}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

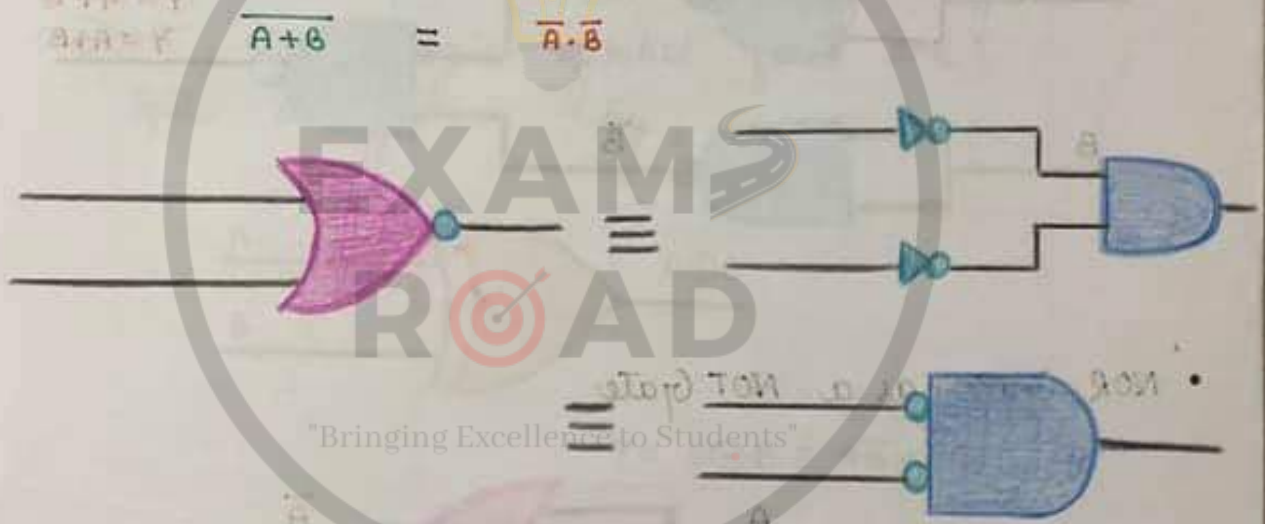


NOR Gate = Bubbled AND Gate

Note: "NAND" and "NOR" are "universal" logic gate. Because we can make all other logic gates by using these logic gates.


• NAND Gate as NOT Gate :

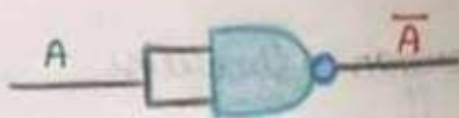

- NAND Gate as AND Gate :

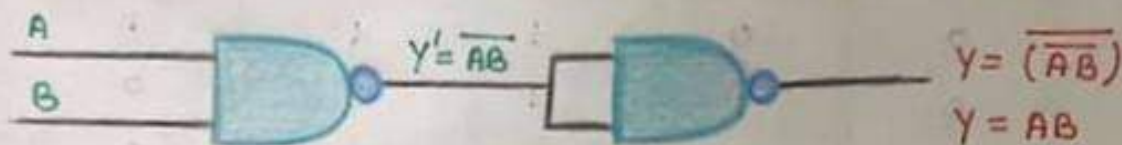


- NAND Gate as OR Gate :

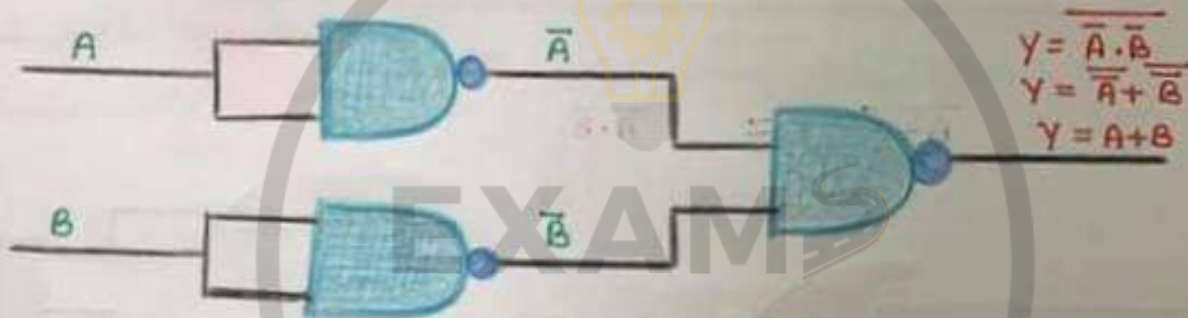

- NOR Gate as a NOT Gate




- NOR Gate as a OR Gate :

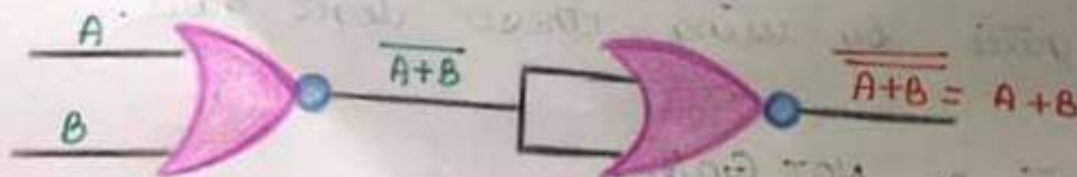




• NOR Gate as AND Gate:

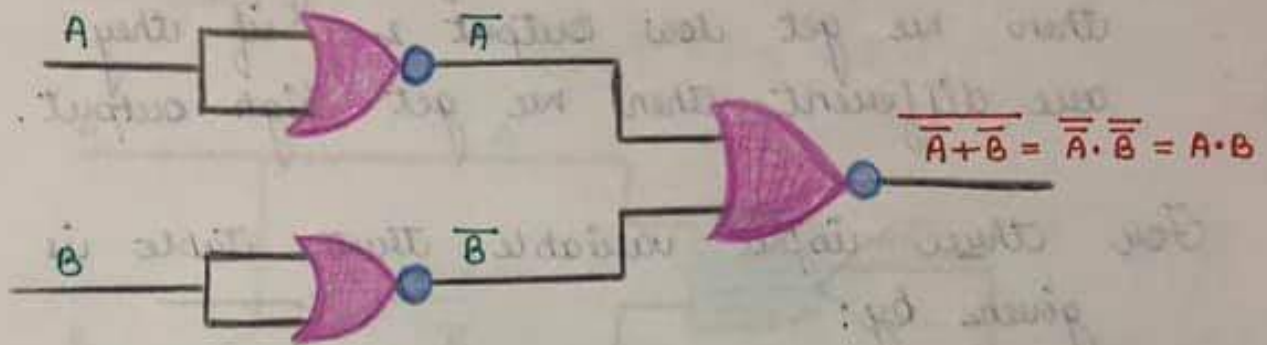

• XOR Gate (Exclusive-OR Gate): (7<sup>th</sup> February 2019) (Thursday)

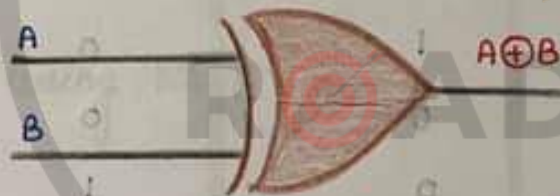A XOR Gate have two or more input but have only single output, the logic symbol for XOR Gate is given by;



"Bringing Excellence to Students"

$$Y = A \oplus B = \overline{A}B + A\overline{B}$$

Truth Table:

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0



For two input variable if they are same then we get low output & if they are different then we get high output.


For three input variable truth table is given by:

A	B	C	$A \oplus B$	$A \oplus B \oplus C$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1


The another logic expression of XOR Gate

$$\begin{aligned}
 Y = A \oplus B &= A\bar{B} + B\bar{A} = (A+B)\bar{A}\bar{B} \\
 &= (A+B)(\bar{A}+\bar{B}) \\
 &= A\bar{A} + A\bar{B} + B\bar{A} + B\bar{B} \\
 &\Rightarrow A\bar{A} = B\bar{B} = 0 \\
 Y &= A\bar{B} + B\bar{A}
 \end{aligned}$$

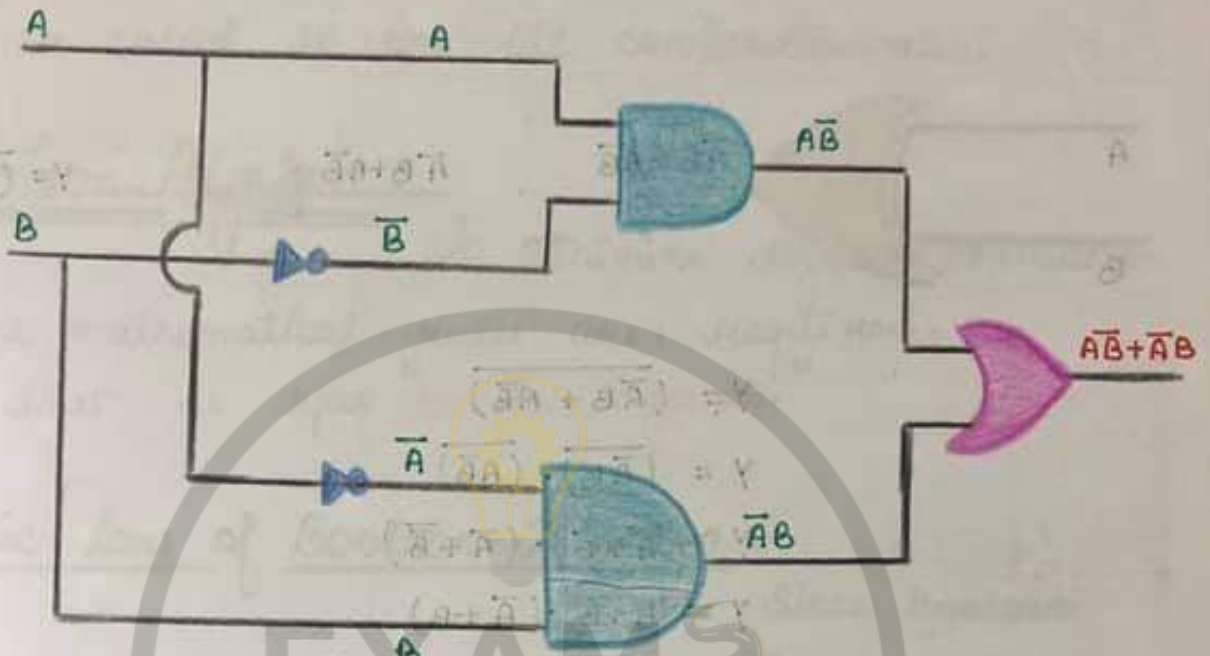*Daughy*  
 Equivalent Circuit of XOR Gate using NOT, AND & OR Gate.




XOR Gate using NAND Gate:

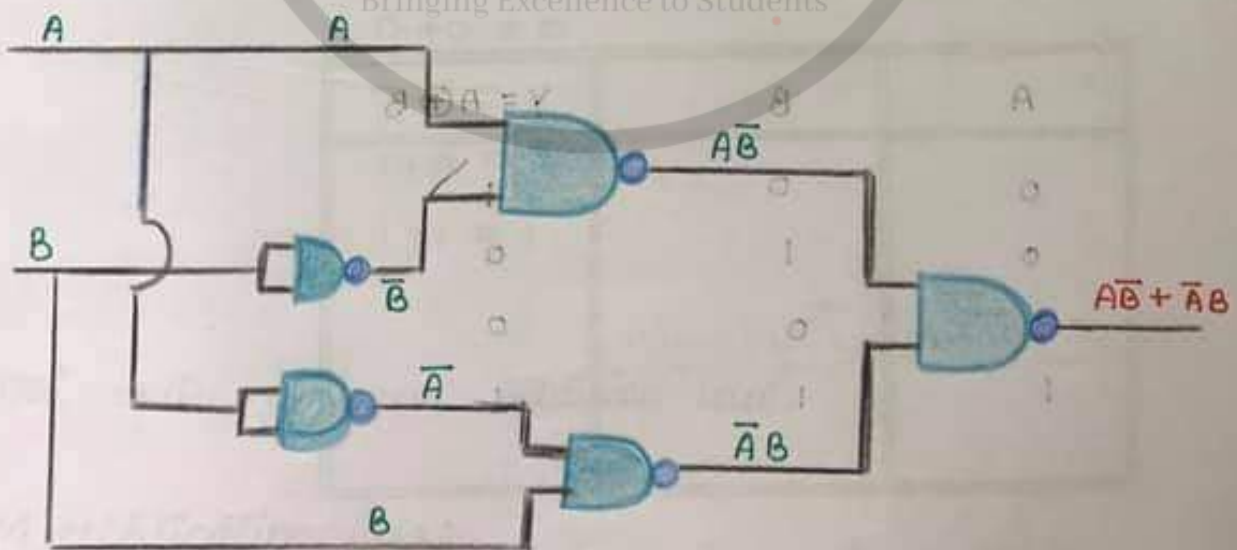



• Exclusive NOR Gate (X-NOR Gate):
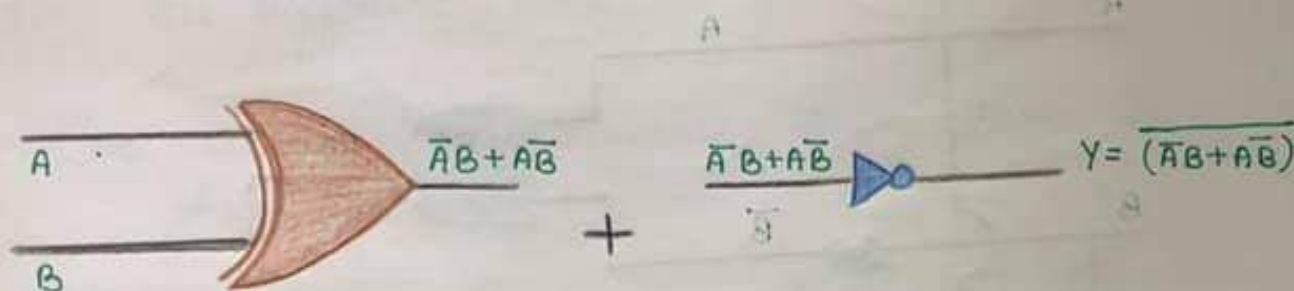
$$X\text{-NOR} = X\text{-OR} + \text{NOT}$$



$$Y = \overline{(\overline{A}B + A\overline{B})}$$

$$Y = (\overline{\overline{A}B}) \cdot (\overline{A\overline{B}})$$

$$Y = (\overline{A} + \overline{B}) \cdot (\overline{A} + \overline{B})$$

$$Y = (A + B) \cdot (\overline{A} + \overline{B})$$

$$Y = A\overline{A} + A\overline{B} + \overline{B}\overline{A} + \overline{B}B$$

$$Y = A\overline{B} + \overline{A}\overline{B}$$

Truth Table:

A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

From truth table output is high only when both input are same [low or high].





If  $A=B$  Then  $Y=1$

If  $A \neq B$  Then  $Y=0$

So, we called it one bit comparator also.

## • Boolean Algebra:

To minimize logical expression some mathematical rules are required, that is k/as "Boolean Algebra".

## • Basic Law of Boolean Algebra:

Since Boolean algebra depend on arithmetic variable & they have value either zero & one.

### → Addition Law:

$$0+0=0$$

$$0+1=1$$

$$1+0=1$$

$$1+1=1$$

'OR' Gate perform Addition Law.

### → Multiplication Law:

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$




Logic Gate have many input but only one output. We can perform arithmetic operation by using Logic Gate Circuit.

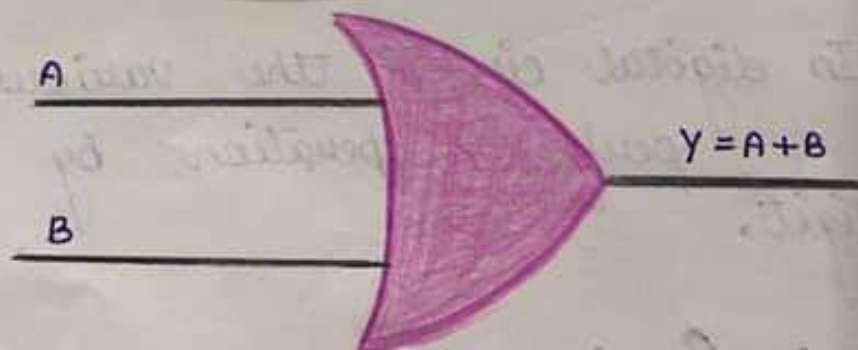Example: AND, OR, NOT, NAND, NOR, X-OR, X-NOR....

• OR-Gate:

OR-Gate have two or more input but have only one output. The output of OR-Gate is high when any one of input is high. If A & B are input variable of OR gate then, output Y is represented by;



"OR" Gate perform Plus (+) operation.





So, Boolean Multiplication is same as AND operation.

## Properties of Boolean Algebra:

Boolean Algebra is a mathematical system which consists of two or more variables and depends on two operations, which are denoted by OR (+) and AND (·).

### Property:

#### → Commutative Property:

Boolean Algebra follows commutative law for both addition and multiplication law.

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

#### → Associative Property:

The associative property for addition & multiplication is given by

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$





→ Distributive Property:

The Boolean Addition is distributive over Boolean multiplication which is given by:

$$A + BC = (A + B)(A + C)$$

$$= A \cdot A + A \cdot C + B \cdot A + B \cdot C$$

$$= A + AC + AB + BC$$

$$= A(1 + C) + AB + BC$$

$$= A + AB + BC$$

$$= A(1 + B) + BC$$

$$= A + BC$$

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

→ Absorption Law:

- $A + AB = A(1 + B) = A$

- $A + \bar{A}B = (A + \bar{A})(A + B)$

$$= (A + B)$$

- $A(A + B) = AA + AB$

$$= A + AB = A(1 + B) = A$$

- $A(\bar{A} + B) = A\bar{A} + AB$

$$= AB$$



→ Idempotent Law :

$$A + A = A, \quad A \cdot A = A$$

→ Double Inversion Law :

$$\overline{\overline{A}} = A$$

OR operation

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + \overline{A} = 1$$

AND operation

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot \overline{A} = 0$$

De-Morgan Theorem :

De Morgan has two statements.

Statement : I

Complement of the sum of A & B is equal to the product of complement of A & B.

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

Statement : II

Complement of product of A & B is equal to the sum of complement of A & B.






Truth Table: (TT: signal output - combination)


A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

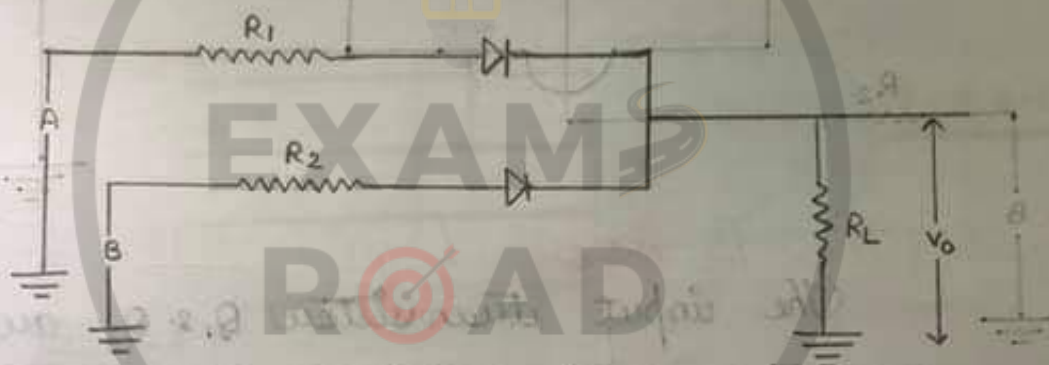OR-Gate Using Diode Logic: (6<sup>th</sup> february '2019) Wednesday




If both input are low then both diode are in reverse bias & will not conduct so, we get "0" output.  
If any 1 input is high then corresponding diode in forward bias & we get high output.

Switching Circuit:

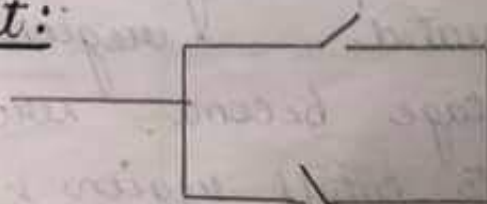



# Transistor - Transistor Logic (TTL)

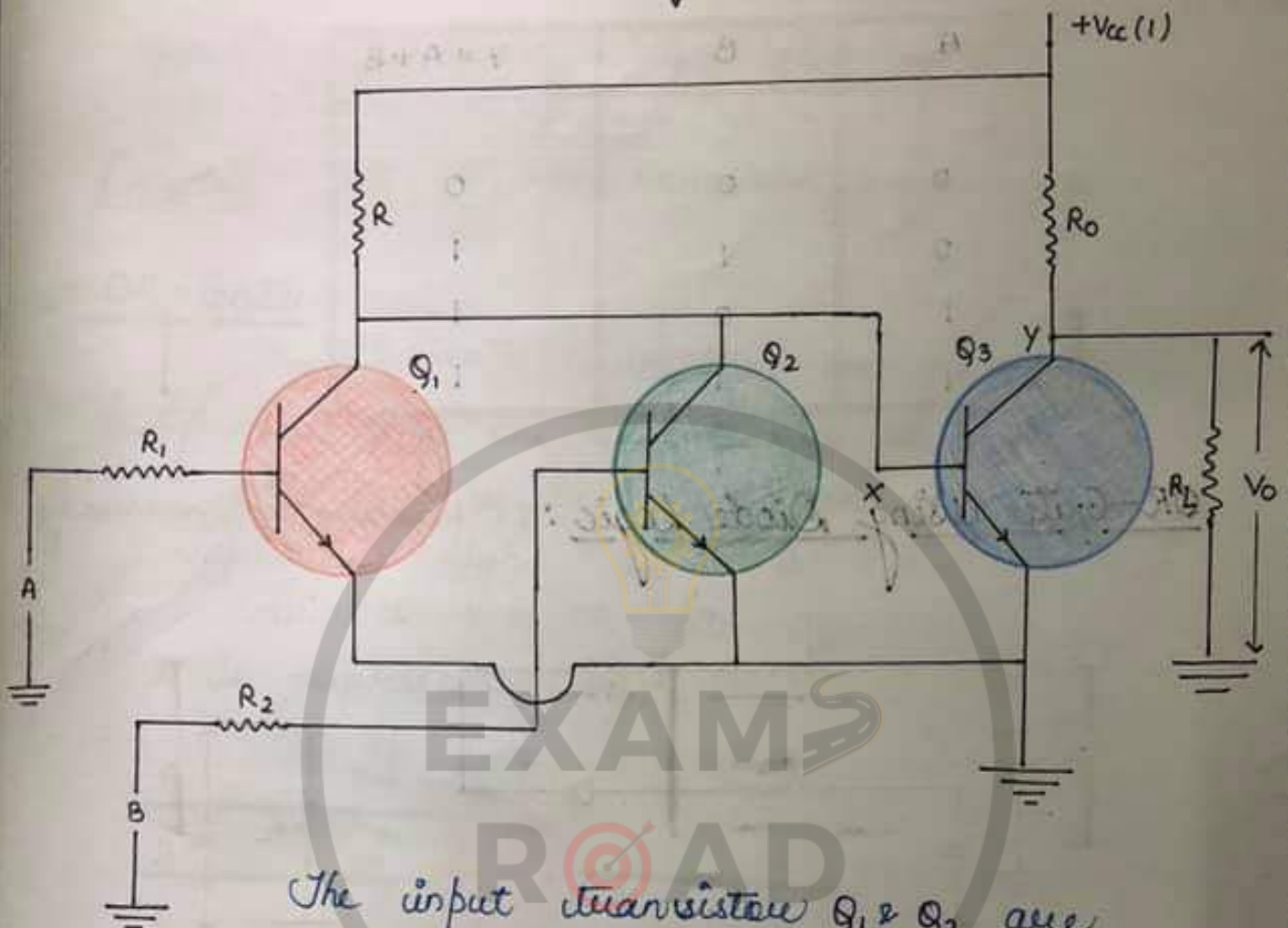

The input transistors  $Q_1$  &  $Q_2$  are connected in series. If both inputs are low then transistors  $Q_1$  &  $Q_2$  are in cutoff region so, voltage at point X is not equal to zero & transistor  $Q_3$  work in saturated region & we get zero output.

If any one of the input is high then corresponding transistor is in saturated region & at point X voltage become zero. So, transistor  $Q_3$  goes into cutoff region & we get high output.



## • AND Gate:


'AND' Gate perform multiply operation. It provide output only when all inputs are high logic [1]. It is represented by;



## Truth Table:


"Bringing Excellence to Students"		
A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

## Switching Circuit:

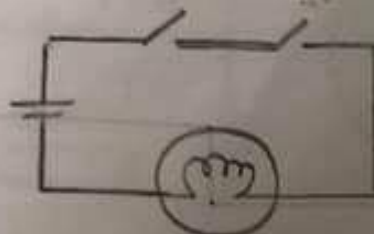




## Diode Logic Circuit:

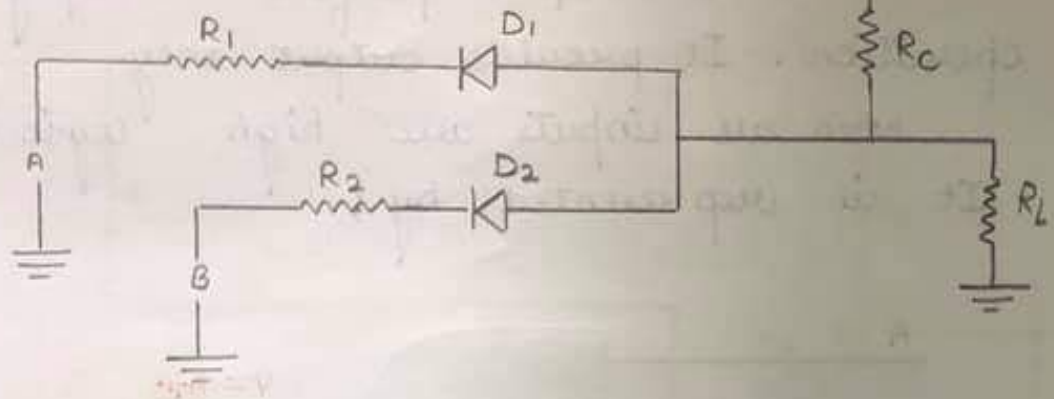

If any input is low then corresponding diode is in forward bias & we get zero output  
if all inputs are high then corresponding all diodes are in reverse bias & we get high output.

## Transistor-Transistor Logic (TTL):

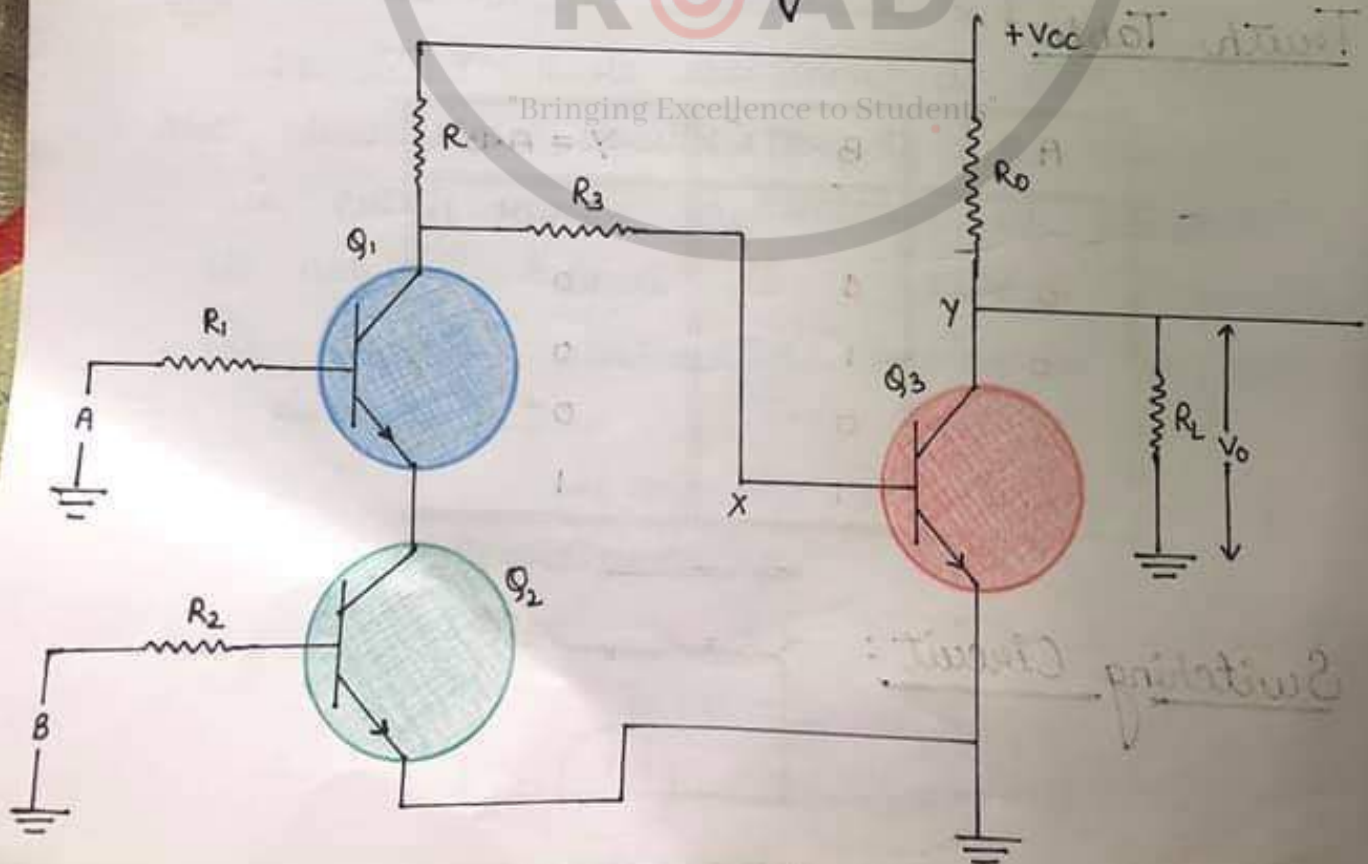



If any one of the input is low then corresponding transistor goes in cutoff region & will not conduct. So, voltage at point X become non-zero & transistor  $Q_3$  goes in saturated region & we get zero output.

If all input are high then corresponding transistor will go in saturated region. So, at point X voltage become zero & transistor  $Q_3$  goes in cutoff region & we get high output.

• NOT Gate:

'NOT' Gate perform reverse operation means when input is low then output is high and vice-versa.

It is represented by;



Truth Table:

A	$Y = \bar{A}$
0	1
1	0